

# Overview

<b>Part I. Device Models and Basic Circuits</b>	<b>1</b>
1. Diode	3
2. Bipolar Transistor	33
3. Field Effect Transistor	169
4. Amplifiers	269
5. Operational Amplifiers	483
6. Latching Circuits	587
7. Logic Families	611
8. Combinatorial Circuits	635
9. Sequential Logic Systems	659
10. Semiconductor Memories	689
<b>Part II. General Applications</b>	<b>723</b>
11. Operational Amplifier Applications	725
12. Controlled Sources and Impedance Converters	767
13. Active Filters	787
14. Signal Generators	843
15. Power Amplifiers	867
16. Power Supplies	885
17. Analog Switches and Sample-and-Hold Circuits	929
18. Digital-Analog and Analog-Digital Converters	945
19. Digital Filters	987
20. Measurement Circuits	1031
21. Sensors and Measurement Systems	1059
22. Electronic Controllers	1103
23. Optoelectronic Components	1127
<b>Part III. Communication Circuits</b>	<b>1147</b>
24. Basics	1149
25. Transmitters and Receivers	1237
26. Passive Components	1283
27. High-Frequency Amplifiers	1321
28. Mixer	1363
29. Appendix	1431
Bibliography	1525
Index	1529

# Contents

<b>Part I. Device Models and Basic Circuits</b>	<b>1</b>
<b>1. Diode</b>	<b>3</b>
1.1 Performance of the Diode	4
1.1.1 Characteristic Curve	4
1.1.2 Description by Equations	5
1.1.3 Switching Performance	8
1.1.4 Small-Signal Response	10
1.1.5 Limit Values and Reverse Currents	11
1.1.6 Thermal Performance	12
1.1.7 Temperature Sensitivity of Diode Parameters	12
1.2 Construction of a Diode	13
1.2.1 Discrete Diode	13
1.2.2 Integrated Diode	15
1.3 Model of a Diode	16
1.3.1 Static Performance	16
1.3.2 Dynamic Performance	19
1.3.3 Small-Signal Model	22
1.4 Special Diodes and Their Application	24
1.4.1 Zener Diode	24
1.4.2 Pin Diode	27
1.4.3 Varactor Diodes	28
1.4.4 Bridge Rectifier	30
1.4.5 Mixer	31
<b>2. Bipolar Transistor</b>	<b>33</b>
2.1 Performance of a Bipolar Transistor	34
2.1.1 Characteristics	34
2.1.2 Description by Way of Equations	36
2.1.3 Characteristic of the Current Gain	37
2.1.4 Operating Point and Small-Signal Response	39
2.1.5 Limit Data and Reverse Currents	45
2.1.6 Thermal Performance	49
2.1.7 Temperature Sensitivity of Transistor Parameters	53
2.2 Design of a Bipolar Transistor	54
2.2.1 Discrete Transistors	55
2.2.2 Integrated Transistors	56

2.3	Models of Bipolar Transistors .....	58
2.3.1	Static Performance .....	58
2.3.2	Dynamic Performance .....	68
2.3.3	Small-Signal Model .....	73
2.3.4	Noise .....	82
2.4	Basic Circuits .....	95
2.4.1	Common-Emitter Circuit .....	96
2.4.2	Common-Collector Circuit .....	131
2.4.3	Common-Base Circuit .....	148
2.4.4	Darlington Circuit .....	159
<b>3.</b>	<b>Field Effect Transistor</b> .....	<b>169</b>
3.1	Behavior of a Field Effect Transistor .....	170
3.1.1	Characteristic Curves .....	172
3.1.2	Description by Equations .....	175
3.1.3	Field Effect Transistor as an Adjustable Resistor .....	179
3.1.4	Operating Point and Small-Signal Behavior .....	181
3.1.5	Maximum Ratings and Leakage Currents .....	185
3.1.6	Thermal Behavior .....	189
3.1.7	Temperature Sensitivity of FET Parameters .....	189
3.2	Construction of the Field Effect Transistor .....	192
3.2.1	Integrated MOSFETs .....	192
3.2.2	Discrete MOSFETs .....	194
3.2.3	Junction FETs .....	197
3.2.4	Cases .....	197
3.3	Models of Field Effect Transistors .....	197
3.3.1	Static Behavior .....	198
3.3.2	Dynamic Behavior .....	206
3.3.3	Small-Signal Model .....	215
3.3.4	Noise .....	222
3.4	Basic Circuits .....	229
3.4.1	Common-Source Circuit .....	230
3.4.2	Common-Drain Circuit .....	252
3.4.3	Common-Gate Circuit .....	261
<b>4.</b>	<b>Amplifiers</b> .....	<b>269</b>
4.1	Circuits .....	271
4.1.1	Current Sources and Current Mirrors .....	277
4.1.2	Cascode circuit .....	312
4.1.3	Differential Amplifier .....	327
4.1.4	Impedance Converters .....	385
4.1.5	Circuits for Setting the Operating Point .....	395
4.2	Properties and Parameters .....	408

4.2.1	Characteristics .....	409
4.2.2	Small-Signal Characteristics .....	412
4.2.3	Nonlinear Parameters .....	426
4.2.4	Noise .....	443
<b>5.</b>	<b>Operational Amplifiers</b> .....	<b>483</b>
5.1	General .....	483
5.1.1	Types of Operational Amplifier .....	484
5.1.2	Principle of Negative Feedback .....	487
5.2	Normal Operational Amplifier (VV-OPA) .....	491
5.2.1	Principle .....	492
5.2.2	Multipurpose Amplifiers .....	494
5.2.3	Operating Voltages .....	497
5.2.4	Single-Supply Amplifiers .....	498
5.2.5	Rail-to-Rail Amplifiers .....	500
5.2.6	Wide-Band Operational Amplifiers .....	504
5.2.7	Frequency Compensation .....	509
5.2.8	Parameters of Operational Amplifiers .....	523
5.3	Transconductance Amplifier (VC-OPA) .....	540
5.3.1	Internal Construction .....	541
5.3.2	Typical Applications .....	543
5.4	Transimpedance Amplifier (CV-OPA) .....	544
5.4.1	Internal Design .....	545
5.4.2	Frequency Response .....	550
5.4.3	Typical Applications .....	551
5.5	The Current Amplifier (CC-OPA) .....	552
5.5.1	The Internal Design .....	552
5.5.2	Typical Applications .....	554
5.6	Comparison .....	568
5.6.1	Practical Implementation .....	570
5.6.2	Types .....	572
<b>6.</b>	<b>Latching Circuits</b> .....	<b>587</b>
6.1	Transistor as Switch .....	587
6.2	Latching Circuits Using Saturated Transistors .....	590
6.2.1	Bistable Circuits .....	591
6.2.2	Monostable Circuits .....	593
6.2.3	Astable Circuits (Multivibrators) .....	594
6.3	Latching Circuits with Emitter-Coupled Transistors .....	595
6.3.1	Emitter-Coupled Schmitt Trigger .....	595
6.3.2	Emitter-Coupled Multivibrator .....	595
6.4	Latching Circuits Using Gates .....	597
6.4.1	Flip-Flops .....	597

6.4.2	One-Shot	597
6.4.3	Multivibrator	598
6.5	Latching Circuits Using Comparators	600
6.5.1	Comparators	600
6.5.2	Schmitt Trigger	601
6.5.3	Multivibrators	604
6.5.4	One-Shots	607
<b>7.</b>	<b>Logic Families</b>	<b>611</b>
7.1	Basic Logic Functions	611
7.2	Construction of Logic Functions	614
7.2.1	Karnaugh Map	615
7.3	Extended Functions	617
7.4	Circuit Implementation of the Basic Functions	618
7.4.1	Resistor-Transistor Logic (RTL)	619
7.4.2	Diode-Transistor Logic (DTL)	620
7.4.3	High-Level Logic (HLL)	620
7.4.4	Transistor-Transistor Logic (TTL)	621
7.4.5	Emitter-Coupled Logic (ECL)	624
7.4.6	Complementary MOS Logic (CMOS)	627
7.4.7	NMOS Logic	631
7.4.8	Summary	631
7.5	Connecting Lines	633
<b>8.</b>	<b>Combinatorial Circuits</b>	<b>635</b>
8.1	Number Representation	636
8.1.1	Positive Integers in Straight Binary Code	636
8.1.2	Positive Integers in BCD Code	637
8.1.3	Binary Integers of Either Sign	637
8.1.4	Fixed-Point Binary Numbers	640
8.1.5	Floating-Point Binary Numbers	640
8.2	Multiplexer – Demultiplexer	643
8.2.1	1-of-n Decoder	643
8.2.2	Demultiplexer	644
8.2.3	Multiplexer	645
8.3	Priority Decoder	646
8.4	Combinatorial Shift Register (Barrel Shifter)	647
8.5	Digital Comparators	648
8.6	Adders	650
8.6.1	Half-Adder	650
8.6.2	Full-Adder	651
8.6.3	Look-Ahead Carry Logic	652
8.6.4	Subtraction	654

8.6.5	Two's-Complement Overflow .....	654
8.6.6	Addition and Subtraction of Floating-Point Numbers .....	655
8.7	Multipliers .....	656
8.7.1	Multiplication of Fixed-Point Numbers .....	656
8.7.2	Multiplication of Floating-Point Numbers .....	658
<b>9.</b>	<b>Sequential Logic Systems</b> .....	<b>659</b>
9.1	Integrated Flip-Flops .....	659
9.1.1	Transparent Flip-Flops .....	659
9.1.2	Flip-Flops with Intermediate Storage .....	661
9.2	Straight Binary Counters .....	666
9.2.1	Asynchronous Straight Binary Counters .....	667
9.2.2	Synchronous Straight Binary Counters .....	667
9.2.3	Up-Down Counters .....	669
9.3	BCD Counters .....	673
9.3.1	Asynchronous BCD Counters .....	673
9.3.2	Synchronous BCD Counters .....	674
9.4	Presetable Counters .....	675
9.5	Shift Registers .....	676
9.5.1	Basic Circuit .....	676
9.5.2	Shift Registers with Parallel Inputs .....	677
9.6	Processing of Asynchronous Signals .....	677
9.6.1	Debouncing of Mechanical Contacts .....	678
9.6.2	Edge-Triggered RS Flip-Flops .....	678
9.6.3	Pulse Synchronization .....	679
9.6.4	Synchronous One-Shot .....	680
9.6.5	Synchronous Edge Detector .....	681
9.6.6	Synchronous Clock Switch .....	681
9.7	Systematic Design of Sequential Circuits .....	682
9.7.1	State Diagram .....	682
9.7.2	Example for a Programmable Counter .....	684
9.8	Dependency notation .....	686
<b>10.</b>	<b>Semiconductor Memories</b> .....	<b>689</b>
10.1	Random Access Memories (RAMs) .....	690
10.1.1	Static RAMs .....	690
10.1.2	Dynamic RAMs .....	693
10.2	RAM Expansions .....	697
10.2.1	Two-Port Memories .....	697
10.2.2	RAMs as Shift Registers .....	698
10.2.3	First-In-First-Out Memories (FIFO) .....	700
10.2.4	Error Detection and Correction .....	702
10.3	Read-Only Memories (ROMs) .....	706

10.3.1	Mask-Programmed ROMs (MROMs) .....	706
10.3.2	Programmable ROMs (PROMs) .....	706
10.3.3	UV-Erasable PROMs (EPROMs) .....	707
10.3.4	Electrically Erasable PROMs (EEPROMs).....	709
10.4	Programmable Logic Devices (PLDs) .....	711
10.4.1	Programmable Logic Array (PAL) .....	714
10.4.2	Computer-Aided PLD Design .....	715
10.4.3	Survey of Types Available.....	717
10.4.4	User Programmable Gate Arrays.....	719

## **Part II. General Applications 723**

<b>11.</b>	<b>Operational Amplifier Applications</b> .....	<b>725</b>
11.1	Summing Amplifier .....	725
11.2	Subtracting Circuits .....	726
11.2.1	Reduction to an Addition .....	726
11.2.2	Subtraction Using a Single Operational Amplifier .....	727
11.3	Bipolar-Coefficient Circuit .....	729
11.4	Integrators .....	730
11.4.1	Inverting Integrator .....	730
11.4.2	Initial Condition .....	733
11.4.3	Summing Integrator.....	734
11.4.4	Noninverting Integrator .....	734
11.5	Differentiators .....	735
11.5.1	Basic Circuit.....	735
11.5.2	Practical Implementation .....	736
11.5.3	Differentiator with High Input Impedance .....	737
11.6	Solving Differential Equations .....	738
11.7	Function Networks .....	739
11.7.1	Logarithm .....	740
11.7.2	Exponential Function .....	743
11.7.3	Computation of Power Functions Using Logarithms .....	744
11.7.4	Sine and Cosine Functions .....	745
11.7.5	Arbitrary Function Networks .....	750
11.8	Analog Multipliers .....	753
11.8.1	Multipliers with Logarithmic Amplifiers.....	753
11.8.2	Transconductance Multipliers.....	754
11.8.3	Multipliers Using Electrically Controlled Resistors.....	759
11.8.4	Adjustment of Multipliers .....	761
11.8.5	Expansion to Four-Quadrant Multipliers .....	761
11.8.6	Multiplier as a Divider or Square Rooter .....	762
11.9	Transformation of Coordinates .....	763

11.9.1	Transformation from Polar to Cartesian Coordinates . . . . .	763
11.9.2	Transformation from Cartesian to Polar Coordinates . . . . .	764
<b>12.</b>	<b>Controlled Sources and Impedance Converters</b>	<b>767</b>
12.1	Voltage-Controlled Voltage Sources . . . . .	767
12.2	Current-Controlled Voltage Sources . . . . .	768
12.3	Voltage-Controlled Current Sources . . . . .	769
12.3.1	Current Sources for Floating Loads . . . . .	769
12.3.2	Current Sources for Grounded Loads . . . . .	771
12.3.3	Precision Current Sources Using Transistors . . . . .	772
12.3.4	Floating Current Sources . . . . .	777
12.4	Current-Controlled Current Sources . . . . .	778
12.5	NIC (Negative Impedance Converter) . . . . .	779
12.6	Gyrator . . . . .	781
12.7	Circulator . . . . .	784
<b>13.</b>	<b>Active Filters</b>	<b>787</b>
13.1	Basic Theory of Lowpass Filters . . . . .	787
13.1.1	Butterworth Lowpass Filters . . . . .	791
13.1.2	Chebyshev Lowpass Filters . . . . .	793
13.1.3	Bessel Lowpass Filters . . . . .	796
13.1.4	Summary of the Theory . . . . .	805
13.2	Lowpass/Highpass Transformation . . . . .	806
13.3	Realization of First-Order Lowpass and Highpass Filters . . . . .	807
13.4	Realization of Second-Order Lowpass and Highpass Filters . . . . .	809
13.4.1	<i>LRC</i> Filters . . . . .	809
13.4.2	Filters with Multiple Negative Feedback . . . . .	809
13.4.3	Filter with Single Positive Feedback . . . . .	810
13.5	Realization of Higher-Order Lowpass and Highpass Filters . . . . .	813
13.6	Lowpass/Bandpass Transformation . . . . .	815
13.6.1	Second-Order Bandpass Filters . . . . .	816
13.6.2	Fourth-Order Bandpass Filters . . . . .	816
13.7	Realization of Second-Order Bandpass Filters . . . . .	819
13.7.1	<i>LRC</i> Bandpass Filter . . . . .	820
13.7.2	Bandpass Filter with Multiple Negative Feedback . . . . .	820
13.7.3	Bandpass Filter with Single Positive Feedback . . . . .	822
13.8	Lowpass/Bandstop Filter Transformation . . . . .	823
13.9	Realization of Second-Order Bandstop Filters . . . . .	824
13.9.1	<i>LRC</i> Bandstop Filter . . . . .	824
13.9.2	Active Parallel-T Bandstop Filter . . . . .	825
13.9.3	Active Wien–Robinson Bandstop Filter . . . . .	825
13.10	Allpass Filters . . . . .	826
13.10.1	Basic Principles . . . . .	826



13.10.2 Realization of First-Order Allpass Filters .....	829
13.10.3 Realization of Second-Order Allpass Filters .....	829
13.11 Adjustable Universal Filters .....	831
13.12 Switched Capacitor Filters .....	836
13.12.1 Principle .....	836
13.12.2 SC Integrator .....	836
13.12.3 First-Order SC Filter .....	837
13.12.4 Second-Order SC Filters .....	838
13.12.5 Implementation of SC Filters with ICs .....	840
13.12.6 General Considerations for Using SC Filters .....	840
13.12.7 A Survey of Available Types .....	840
<b>14. Signal Generators .....</b>	<b>843</b>
14.1 LC Oscillators .....	843
14.1.1 Condition for Oscillation .....	843
14.1.2 Meissner Oscillator .....	845
14.1.3 Hartley Oscillator .....	846
14.1.4 Colpitts Oscillator .....	847
14.1.5 Emitter-Coupled LC Oscillator .....	847
14.1.6 Push–Pull Oscillators .....	848
14.2 Crystal Oscillators .....	849
14.2.1 Electrical Characteristics of a Quartz Crystal .....	849
14.2.2 Fundamental Frequency Oscillators .....	850
14.2.3 Harmonic Oscillators .....	852
14.3 Wien–Robinson Oscillator .....	853
14.4 Differential-Equation Oscillators .....	857
14.5 Function Generators .....	859
14.5.1 Basic Arrangement .....	860
14.5.2 Practical Implementation .....	861
14.5.3 Function Generators with a Controllable Frequency .....	862
14.5.4 Simultaneously Producing Sine and Cosine Signals .....	864
<b>15. Power Amplifiers .....</b>	<b>867</b>
15.1 Emitter Follower as a Power Amplifier .....	867
15.2 Complementary Emitter Followers .....	869
15.2.1 Complementary Class-B Emitter Follower .....	869
15.2.2 Complementary Class-AB Emitter Followers .....	871
15.2.3 Generation of the Bias Voltage .....	872
15.3 Complementary Darlington Circuits .....	874
15.4 Complementary Source Followers .....	875
15.5 Current Limitation .....	876
15.6 Four-Quadrant Operation .....	878
15.7 Design of a Power Output Stage .....	879

15.8	Driver Circuits with Voltage Gain .....	882
15.9	Boosting the Output Current of Integrated Operational Amplifiers .....	884
<b>16.</b>	<b>Power Supplies</b> .....	<b>885</b>
16.1	Properties of Power Transformers .....	885
16.2	Power Rectifiers .....	886
16.2.1	Half-Wave Rectifier .....	886
16.2.2	Bridge Rectifier .....	887
16.2.3	Center-Tap Rectifier .....	891
16.3	Linear Voltage Regulators .....	892
16.3.1	Basic Regulator .....	892
16.3.2	Voltage Regulators with a Fixed Output Voltage .....	893
16.3.3	Voltage Regulators with an Adjustable Output Voltage .....	895
16.3.4	A Voltage Regulator with a Reduced Dropout Voltage .....	896
16.3.5	A Voltage Regulator for Negative Voltages .....	897
16.3.6	Symmetrical Division of a Floating Voltage .....	898
16.3.7	Voltage Regulator with Sensor Terminals .....	899
16.3.8	Bench Power Supplies .....	900
16.3.9	IC Voltage Regulators .....	901
16.4	Reference Voltage Generation .....	901
16.4.1	Zener Diode References .....	901
16.4.2	Bandgap Reference .....	904
16.4.3	Types .....	906
16.5	Switched-Mode Power Supplies .....	907
16.6	Secondary Switching Regulators .....	908
16.6.1	Step-Down Converters .....	908
16.6.2	Generating the Switching Signal .....	911
16.6.3	Step-Up Converters .....	913
16.6.4	Inverting Converter .....	914
16.6.5	Charge Pump Converter .....	914
16.6.6	Integrated Switching Regulators .....	915
16.7	Primary Switching Regulators .....	916
16.7.1	Single-Ended Converters .....	917
16.7.2	Push-Pull Converters .....	918
16.7.3	High-Frequency Transformers .....	920
16.7.4	Power Switches .....	921
16.7.5	Generating the Switching Signals .....	924
16.7.6	Loss Analysis .....	925
16.7.7	IC Drive Circuits .....	926
<b>17.</b>	<b>Analog Switches and Sample-and-Hold Circuits</b> .....	<b>929</b>
17.1	Principle .....	929

17.2	Electronic Switches .....	930
17.2.1	FET Switch .....	930
17.2.2	Diode Switch .....	933
17.2.3	Bipolar Transistor Switch .....	935
17.2.4	Differential Amplifier Switch .....	937
17.3	Analog Switches Using Amplifiers .....	939
17.3.1	Analog Switches for High Voltages .....	940
17.3.2	Amplifier with Switchable Gain .....	940
17.4	Sample-and-Hold Circuits .....	941
17.4.1	Basic Principles .....	941
17.4.2	Practical Implementation .....	943
<b>18.</b>	<b>Digital-Analog and Analog-Digital Converters</b> .....	<b>945</b>
18.1	Sampling Theorem .....	945
18.1.1	Practical Aspects .....	947
18.2	Resolution .....	950
18.3	Principles of D/A Conversion .....	951
18.4	D/A Converters in CMOS Technology .....	952
18.4.1	Summation of Weighted Currents .....	952
18.4.2	D/A Converters with Double-Throw Switches .....	952
18.4.3	Ladder Network .....	953
18.4.4	Inverse Operation of a Ladder Network .....	954
18.5	A Ladder Network for Decade Weighting .....	955
18.6	D/A Converters in Bipolar Technology .....	956
18.7	D/A Converters for Special Applications .....	958
18.7.1	Processing Signed Numbers .....	958
18.7.2	Multiplying D/A Converters .....	960
18.7.3	Dividing D/A Converters .....	960
18.7.4	D/A Converter as Function Generator .....	961
18.8	Accuracy of DA Converters .....	963
18.8.1	Static Errors .....	963
18.8.2	Dynamic Characteristics .....	964
18.9	Principles of A/D Conversion .....	966
18.10	Design of A/D Converters .....	967
18.10.1	Parallel Converter .....	967
18.10.2	Two Step Converters .....	969
18.10.3	Successive Approximation .....	972
18.10.4	Counting Method .....	975
18.10.5	Oversampling .....	979
18.11	Errors in AD-Converters .....	983
18.11.1	Static Errors .....	983
18.11.2	Dynamic Errors .....	984
18.12	Comparison of AD-Converters .....	985

<b>19. Digital Filters</b>	<b>987</b>
19.1 Digital Transfer Function	988
19.1.1 Time Domain Analysis	988
19.1.2 Frequency Domain Analysis	988
19.2 Basic Structures	991
19.3 Design Analysis of FIR Filters	994
19.3.1 Basic Equations	995
19.3.2 Simple Examples	996
19.3.3 Calculating the Filter Coefficients	1000
19.4 Realization of FIR Filters	1013
19.4.1 Realization of FIR Filters Using the Parallel Method	1014
19.4.2 Realization of FIR Filters Using the Serial Method	1014
19.5 Design of IIR Filters	1015
19.5.1 Calculating the Filter Coefficients	1016
19.5.2 IIR Filters in a Cascade Structure	1018
19.6 Realization of IIR Filters	1022
19.6.1 Construction from Simple Building Blocks	1022
19.6.2 Design Using LSI Devices	1025
19.7 Comparison of FIR and IIR Filters	1027
<b>20. Measurement Circuits</b>	<b>1031</b>
20.1 Measurement of Voltage	1031
20.1.1 Impedance Converter	1031
20.1.2 Measurement of Potential Difference	1032
20.1.3 Isolation Amplifiers	1037
20.2 Measurement of Current	1040
20.2.1 Floating Zero-Resistance Ammeter	1040
20.2.2 Measurement of Current at High Potentials	1041
20.3 AC/DC Converters	1042
20.3.1 Measurement of the Mean Absolute Value	1042
20.3.2 Measurement of the rms Value	1046
20.3.3 Measurement of the Peak Value	1050
20.3.4 Synchronous Demodulator	1053
<b>21. Sensors and Measurement Systems</b>	<b>1059</b>
21.1 Temperature Measurement	1059
21.1.1 Metals as PTC Thermistors	1062
21.1.2 Silicon-Based PTC Thermistors	1062
21.1.3 NTC Thermistors	1063
21.1.4 Operation of Resistive Temperature Detectors	1063
21.1.5 Transistors as Temperature Sensors	1068
21.1.6 Thermocouple	1071
21.1.7 An Overview of Types	1075

21.2	Pressure Measurement . . . . .	1076
21.2.1	Design of Pressure Sensors . . . . .	1077
21.2.2	The Operation of Temperature-Compensated Pressure Sensors .	1079
21.2.3	Temperature Compensation for Pressure Sensors . . . . .	1082
21.2.4	Commercially Available Pressure Sensors . . . . .	1085
21.3	Humidity Measurement . . . . .	1086
21.3.1	Humidity Sensors . . . . .	1087
21.3.2	Interfacing Circuits for Capacitive Humidity Sensors . . . . .	1088
21.4	The Transmission of Sensor Signals . . . . .	1090
21.4.1	Electrical (Direct-Coupled) Signal Transmission . . . . .	1090
21.4.2	Electrically Isolated Signal Transmission . . . . .	1093
21.5	Calibration of Sensor Signals . . . . .	1094
21.5.1	Calibration of the Analog Signal . . . . .	1095
21.5.2	Computer-Aided Calibration . . . . .	1098
<b>22.</b>	<b>Electronic Controllers</b>	<b>1103</b>
22.1	Underlying Principles . . . . .	1103
22.2	Controller Types . . . . .	1104
22.2.1	P-controller . . . . .	1104
22.2.2	PI-Controller . . . . .	1106
22.2.3	PID-Controller . . . . .	1108
22.2.4	The PID-Controller with Adjustable Parameters . . . . .	1110
22.3	Control of Nonlinear Systems . . . . .	1112
22.3.1	Static Nonlinearity . . . . .	1112
22.3.2	Dynamic Nonlinearity . . . . .	1113
22.4	Phase-Locked Loop . . . . .	1114
22.4.1	Sample-and-Hold Circuit as a Phase Detector . . . . .	1116
22.4.2	Synchronous Demodulator as a Phase Detector . . . . .	1118
22.4.3	The Frequency-Sensitive Phase Detector . . . . .	1120
22.4.4	The Phase Detector with an Extensible Measuring Range . . . . .	1122
22.4.5	The PLL as a Frequency Multiplier . . . . .	1123
<b>23.</b>	<b>Optoelectronic Components</b>	<b>1127</b>
23.1	Basic Photometric Terms . . . . .	1127
23.2	Photoconductive Cells . . . . .	1129
23.3	Photodiodes . . . . .	1130
23.4	Phototransistors . . . . .	1132
23.5	Light-Emitting Diodes . . . . .	1133
23.6	Optocouplers . . . . .	1134
23.7	Visual Displays . . . . .	1134
23.7.1	Binary Displays . . . . .	1135
23.7.2	Analog Displays . . . . .	1136
23.7.3	Numerical Displays . . . . .	1138

23.7.4	Multiplex Displays .....	1139
23.7.5	Alphanumeric Displays .....	1141

**Part III. Communication Circuits 1147**

<b>24.</b>	<b>Basics</b> .....	<b>1149</b>
24.1	Telecommunication Systems .....	1149
24.2	Transmission Channels .....	1152
24.2.1	Cable .....	1152
24.2.2	Radio Communication .....	1163
24.2.3	Fibre Optic Links .....	1168
24.2.4	Comparison of Transmission Channels .....	1173
24.3	Reflection Coefficient and S Parameters .....	1174
24.3.1	Wave Parameters .....	1174
24.3.2	Reflection Coefficient .....	1175
24.3.3	Wave Source .....	1181
24.3.4	S Parameters .....	1183
24.4	Modulation Methods .....	1191
24.4.1	Amplitude Modulation .....	1194
24.4.2	Frequency Modulation .....	1202
24.4.3	Digital Modulation Methods .....	1209
24.5	Multiple Use and Grouping of Communication Channels .....	1227
24.5.1	Multiplex Operation .....	1227
24.5.2	Duplex Operation .....	1234
<b>25.</b>	<b>Transmitters and Receivers</b> .....	<b>1237</b>
25.1	Transmitters .....	1237
25.1.1	Transmitters with Analogue Modulation .....	1237
25.1.2	Transmitters with Digital Modulation .....	1243
25.1.3	Generating Local Oscillator Frequencies .....	1244
25.2	Receivers .....	1245
25.2.1	Direct-Detection Receivers .....	1246
25.2.2	Superheterodyne Receivers .....	1247
25.2.3	Gain Control .....	1253
25.2.4	Dynamic Range of a Receiver .....	1259
25.2.5	Receivers for Digital Modulation .....	1265
<b>26.</b>	<b>Passive Components</b> .....	<b>1283</b>
26.1	High-Frequency Equivalent Circuits .....	1283
26.1.1	Resistor .....	1284
26.1.2	Inductor .....	1286
26.1.3	Capacitor .....	1288
26.2	Filters .....	1289

26.2.1	LC-Filters	1290
26.2.2	Dielectric Filters	1296
26.2.3	SAW Filters	1298
26.3	Circuits for Impedance Transformation	1301
26.3.1	Impedance Matching	1301
26.3.2	Coupling	1311
26.4	Power Splitters and Hybrids	1314
26.4.1	Power Splitter	1315
26.4.2	Hybrids	1316
<b>27.</b>	<b>High-Frequency Amplifiers</b>	<b>1321</b>
27.1	Integrated High-Frequency Amplifiers	1321
27.1.1	Impedance Matching	1322
27.1.2	Noise Figure	1324
27.2	High-Frequency Amplifiers with Discrete Transistors	1327
27.2.1	Generalized Discrete Transistor	1327
27.2.2	Setting the Operating Point (Biasing)	1329
27.2.3	Impedance Matching for a Single-Stage Amplifier	1332
27.2.4	Impedance Matching in Multi-stage Amplifiers	1338
27.2.5	Neutralization	1340
27.2.6	Special Circuits for Improved Impedance Matching	1343
27.2.7	Noise	1346
27.3	Broadband Amplifiers	1349
27.3.1	Principle of a Broadband Amplifier	1349
27.3.2	Design of a Broadband Amplifier	1351
27.4	Power Gain	1354
27.4.1	Direct Power Gain	1355
27.4.2	Insertion Gain	1356
27.4.3	Transfer Gain	1357
27.4.4	Available Power Gain	1358
27.4.5	Comparison of Gain Definitions	1358
27.4.6	Gain with Impedance Matching at Both Sides	1359
27.4.7	Maximum Power Gain with Transistors	1360
<b>28.</b>	<b>Mixer</b>	<b>1363</b>
28.1	Functional Principle of an Ideal Mixer	1363
28.1.1	Up-Conversion Mixer	1364
28.1.2	Down-Conversion Mixer	1365
28.2	Functional Principles of Practical Mixers	1367
28.2.1	Additive Mixing	1367
28.2.2	Multiplicative Mixers	1376
28.3	Mixers with Diodes	1381
28.3.1	Unbalanced Diode Mixer	1381

28.3.2	Single Balanced Diode Mixers .....	1391
28.3.3	Double Balanced Diode Mixer .....	1395
28.3.4	Diode Mixers in Practical Use .....	1401
28.4	Mixers with Transistors .....	1404
28.4.1	Single Balanced Mixer .....	1404
28.4.2	Double Balanced Mixer (Gilbert Mixer) .....	1417
<b>29.</b>	<b>Appendix</b>	<b>1431</b>
29.1	PSpice – Brief User’s Guide .....	1431
29.1.1	General .....	1431
29.1.2	Programs and Files .....	1431
29.1.3	A Simple Example .....	1434
29.1.4	Further Examples .....	1450
29.1.5	Integrating Other Libraries .....	1455
29.1.6	Some Typical Errors .....	1457
29.2	ispLEVER – Brief User’s Guide .....	1459
29.2.1	Outline .....	1459
29.2.2	Circuit Entry .....	1461
29.2.3	Pin Assignment .....	1475
29.2.4	Simulation .....	1479
29.2.5	Optimization .....	1484
29.2.6	Programming .....	1484
29.2.7	Outlook .....	1487
29.3	Passiv RC and LRC Networks .....	1488
29.3.1	The Lowpass Filter .....	1488
29.3.2	The Highpass Filter .....	1491
29.3.3	Compensated Voltage Divider .....	1494
29.3.4	Passive <i>RC</i> Bandpass Filter .....	1495
29.3.5	Wien–Robinson Bridge .....	1495
29.3.6	Parallel-T Filter .....	1497
29.3.7	Resonant Circuit .....	1498
29.4	Definitions and Nomenclature .....	1500
29.5	Types of the 7400 Digital Families .....	1508
29.6	Standard Series .....	1515
29.7	Color code .....	1516
29.8	Manufacturers .....	1518
	<b>Bibliography</b>	<b>1525</b>
	<b>Index</b>	<b>1529</b>