

Index

- A/D conversion 968
- AB push-pull 548, 556, 779
- absolute humidity 1088
- absolute pressure sensor 1080
- absorption law 613
- AC coupling 117, 122, 140
- AC Sweep 1442
- AC/DC converter 1044
- acceleration 1063
- accuracy 965
- acquisition time 943
- active
 - filter 789, 836
 - rectifier 929
 - termination 565
- adapted frequency compensation 516
- adaptive filter 1031
- ADC 968
- adders 652
- additive mixing 1369, 1374
- address
 - time 695
 - setup time 695
- adjustable universal filter 833
- adjustment of multipliers 763
- aliasing 949, 1277, 1280
- allpass
 - filter 828
 - filter coefficient 830
- alphanumeric display 1143
- Alumel 1075
- ambient temperature 882
- amplifier 271, 1323
 - characteristics 411, 414
 - distortion 432
 - intermodulation 436
 - model 416
 - noise 445, 449, 540, 1326
 - parameters 415
 - series connection 423, 441, 451
 - variable gain 1255, 1257
- amplitude
 - condition 512
 - control 860
 - modulation 1193, 1196
 - modulator 1200
 - shift keying (ASK) 1195, 1212
- amplitude-dependent current limitation 879
- analog
 - multiplexer 935
 - multiplier 755, 1057
 - switch 931, 934, 942
 - transversal 1225
- analog-digital converter 947
- analysis 1434
- AND gate 631
- anemometer 1063
- angle 1063
 - modulation 1193
- anode 3
- antenna 1165
- antifuse 722
- antivalence 619
- aperture
 - delay 944
 - jitter 987
- apparent power 1505
- arbitrary coefficient 833
- arithmetic
 - logic units (ALUs) 656
 - mean 1492
- ASCII character generator 1145
- associative law 613
- astable 592, 596, 608
- asynchronous 669
- attenuation 1159, 1169, 1175
 - constant 1157
- attributes 1438
- available power 1184
 - gain 453, 1360, 1362
- averaging 1492

- balanced diode mixer 1393
- band pass filter 1292
- band-stop filter 825, 1000, 1011
- bandgap
 - reference 906, 1071
 - voltage 12, 55
- bandpass 841
 - filter 817, 821, 824, 835, 1011, 1022, 1292, 1497
- bandstop filter 825, 827, 835, 1023
- bandwidth 537, 1217
 - efficiency 1219
- bar 1079
- bar-graph display 1139
- Bartlett symmetry theorem 347
- barrel-shifter 649
- base 35

- spreading resistance 69
- station 1230
- baseband 1193
 - signal 1215, 1216
- basic circuit 96, 231, 232
- BCD
 - code 639
 - counter 675, 676
- bench power supply 902
- Bessel 790
 - characteristic 1296
 - filters 798, 802
 - function 1206
 - polynomials 799
- bias voltage 874
- biasing 1331
- bilinear transformation 1018, 1019, 1022
- binary
 - counter 670
 - integers 639
- bipolar
 - coefficient 731
 - output 961
 - output current 777
 - transistor 35
- biquad-filter 835, 840, 859
- bistable 592, 593
- Blackman window 1003
- Bode
 - diagram 515
 - plot 1106, 1111, 1490
- Boltzmann's constant 12, 55, 85
- bond wire 14
- Boolean algebra 613
- boost
 - capacitor 915
 - converter 918
- Booth algorithm 659
- boundary ccan 1487
- branching state 685
- breakdown
 - characteristic 48
 - voltage 47, 48
- breakpoint 748
- breakthrough 18
 - current 16
 - voltage 4, 11
- bridge rectifier 15, 30, 889
- broadband amplifiers 1351
- broadcasting 1170, 1229
- Buck converter 918
- building block 1024
- bulk diodes 195
- Burst refresh 698
- Butterworth 790, 793
 - characteristic 1294
 - filters 803
- polynomials 794
- cable 1154, 1160
- calibration 1096
- capacitances
 - junction 211
 - overlap 208, 211
- capacitive
 - humidity sensor 1089
 - load 521
- capacitor 1285, 1290
- capture range 1120
- carrier 1193
- carry 652
- Carson bandwidth 1207
- cartesian to polar 766
- cascade 671
 - structure 1011, 1020
- cascode
 - circuit 314, 478, 507
 - current mirror 298
 - differential amplifier 357, 365
- case
 - model 1190
 - temperature 50
- cathode 3
- Cauer 796
- CC operational 555
- CDMA 1231
- center-tap rectifier 893
- channel 171, 1151
 - filter 1267
- character generator 1145
- characteristic impedance 1161
- characteristics
 - output 189
 - transfer 176
- charge pump 917
 - converter 916, 917
- charge-coupled device (CCD) 1224
- Chebyshev 790, 795
 - characteristic 1295
 - filter 804
 - polynomials 795
- check bit 704
 - error 707
- chip select 693
- Chromel 1075
- circuit
 - common-drain 254, 256
 - common-gate 263, 267
 - diagram 1472
 - entry 1463
 - symbol 615
- circulator 786, 1345
- clamping amplifiers 573
- class AB operation 509

- class-A operation 870
- class-AB emitter follower 873
- class-B operation 871
- clock 662, 663, 670, 685
- clocked *RS* flip-flop 662
- CMOS 194
 - inverter 629
 - operational amplifiers 502
- CMRR 331
- coaxial cable 546, 635, 1154
- code division multiple access 1231
- coefficient 1007, 1013
 - multiplier 995
 - transconductive 201
- coincidence 673
- collector 35
 - capacitance 79
 - spreading resistance 69
- Collins
 - filter 463, 1307, 1343
 - transformer 463
- color code 1518
- Colpitts oscillator 849, 855, 1208
- column
 - address strobe 696
 - decoder 693, 696
- combinatorial
 - circuits 637
 - shift register (barrel shifter) 649
- common-base circuit 150, 558
- common-collector circuit 133, 387, 395, 477, 558
- common-drain circuit 388, 397, 471, 477
- common-emitter circuit 97, 102, 132, 476, 557
- common-gate circuit 472
- common-mode
 - gain 330, 348, 375, 527
 - rejection 527, 728, 729
 - rejection cutoff frequency 377
 - rejection ratio 331
 - voltage 494
- common-source 232, 234, 476
- commutative law 613
- comparator 602, 650, 970
- complementary
 - cascode differential amplifier (folded cascode) 508
 - Darlington circuits 876
 - emitter follower 871
 - impedance converters 391
 - MOS Logic (CMOS) 629
 - source follower 877
- complex PLD 720
- compression point 434
- computer-aided calibration 1100
- configurable logic blocks, CLBs 721
- connecting lines 635
- constantan 1075
- constellation diagram 1218, 1221
- constraint editor 1480
- controlled
 - cascode current mirror 313
 - coefficient 761
 - resistor 761, 836
 - source 769
 - system 1105
 - variable 1105
- conventional oversampling 982
- conversion
 - gain 1374, 1390, 1414
 - loss 1374, 1404
- converter, current-to-voltage 243, 252
- cooling 573
- copper losses 928
- copper–constantan thermocouple 1073
- correcting variable 1105
- cosine
 - filter 1226
 - function 747, 751
 - roll-off
 - pulses 1221
- counter 668
 - method 977
- counting method 953, 968
- coupling 1313
 - network 1495
- CPLDs 720, 1463
- crest factor 1048, 1272
- critical
 - damping 790
 - frequency 513
- critically coupled 1294
- critically damped filter 801
- crossover distortion 873, 884
- crystal oscillator 851, 853, 1062
- Cuk converter 918
- current 1502
 - amplifier 487, 488, 554
 - biasing 118
 - booster 886
 - feedback 103, 119, 236, 250, 465, 467, 488, 1331
 - gain 37, 39, 40, 67, 80, 164, 167
 - limitation 878
 - loop 1094
 - loop transmitter 1095
 - mirror 279, 399, 780
 - mirror with cascode 296
 - on demand 510, 556
 - source 279, 473, 1503
 - source bank 289
- current-controlled
 - current source 780

- voltage source 770
- current-time area 11
- current-to-voltage converter 115, 151
- cutoff
 - current 49
 - frequency 83, 124, 320, 514, 1490
 - region 35
- cycle stealing 698, 699

- D flip-flops 662
- damping 573
- Darlington
 - circuit 161, 389
 - transistor 161, 168
- data
 - error 707
 - lockout 665
 - rate 1218
 - retention 696
- DC
 - coupling 123, 140
 - sweep 1442
- DC-coupled 485
- DC/DC converter 910
- De Morgans 614
- debouncing 680
- decoder 645
- DECT 1170
- deglitchers 968
- delay
 - element 990, 991, 995
 - time 591
- $\Delta\Sigma$
 - converter 982
 - modulator 982
- demodulation 1058, 1201, 1208
- demodulator 1058, 1151, 1215
- demultiplexer 645, 646, 932
- dependency notation 688
- depletion 171
- device fitter 719, 722
- diamond transistor 488, 556
- diaphragm 1079
- dielectric
 - constant 178
 - filter 1292, 1298
 - insulation 934
- die 13
- difference equation 992
- differential
 - amplifier 329, 351, 478, 559, 626, 750, 1407
 - amplifier with a current mirror 358
 - amplifier with cascode current sources 355
 - amplifier with current feedback 337, 341, 361
 - amplifier with simple current sources 353
 - amplifier with symmetric output 342
 - discriminator 1210
 - equation 740
 - gain 331, 494, 527
 - nonlinearity 986
 - output amplifiers 585
 - pressure sensor 1080
 - quadri-phase shift keying (DQPSK) 1220
 - resistance 10, 22
 - signaling 636
 - switch 939
 - equation oscillator 859
- differentiating 1495
- differentiator 737, 1000
- diffusion
 - capacitance 20, 72
 - current 16
 - range 16
 - voltage 17
- digit at a time 968
- digital 589
 - analog converter 947
 - channel filter 1269
 - demodulator 1215
 - families 1510
 - filter 982, 989
 - gain control 1260
 - modulation 1211, 1245
 - modulator 1214
 - sample and hold 970
 - signal processor (DSPs) 1030
 - transfer function 992
 - transmitter 1245
 - voltmeter 985
- diode 3, 277
 - substrate 202
 - bridge 936
 - mixer 1383, 1397
 - switch 935
 - transistor logic (DTL) 622
- Dirac impulse 947
- direct
 - conversion receiver 1279
 - feedback 564
 - modulation 1239
- direct-detection receiver 1248
- direct-detector 1248
- directivity 1166
- discrete transistor 57
- discriminator 1208
- disjunctive normal form 616
- display 1136
- dissipation 573
 - capacitance 634
- distortion factor 47, 103, 108, 235, 239, 361, 432, 442
- distributed adder 994

- distributive law 613
- disturbance 1105
- divider 760, 764
- dividing D/A converter 962
- division 759
- DMOS 196
- dot matrix display 1144
- dot-position display 1139
- double
 - balanced mixer 1406, 1419
 - cascode current mirror 309
 - center-tag rectifier 893
 - precision 644
 - sideband modulation 1197
- down-conversion 1365
- downconverter 31
- downlink 1234, 1266
- drain 171
- drive-R amplifier 488, 565
- dropout voltage 898
- dual transformation 786
- dual-gate MOSFET 1376
- dual-slope converter 979
- dual-transform 783
- duplexer 1166, 1237, 1266
- duty cycle 865, 910
- dynamic
 - error 986
 - losses 927
 - nonlinearity 1115
 - RAM 695, 697
 - RAM controller 698
 - range 1261, 1266, 1271
- Early
 - effect 38, 65
 - voltage 38
- Ebers–Moll model 60
- edge detector 683
- edge-triggered flip-flops 665
- EEPROMs 711
- effect
 - narrow-channel 203
 - short-channel 203
 - sub-threshold 200, 203
- effective power 1505
- efficiency 869, 909, 1131
- electromagnetic compatibility 1171
- electrometer amplifier 1035
- electronic
 - control 835
 - controller 1105
- elementary charge 12, 55
- Elliptic filter 796
- emission
 - coefficient 16
 - factor 204
- emitter 35
 - capacitance 79
 - follower 133, 869
 - spreading resistance 69
 - coupled 597
 - coupled logic (ECL) 626
 - coupled oscillator 849, 855
- enhancement 171
- envelope
 - detection 1197
 - detector 1201, 1209
- EPROMs 709
- equal ripple 795
- equation, small-signal 184
- equivalence 619
- equivalent, small-signal 186
 - circuit 7
 - diode circuit 35
 - noise 464
 - noise bandwidth 483
 - noise current source 88
 - noise source 88, 445
 - noise voltage source 88
 - series inductance (ESL) 914
 - series resistance (ESR) 914
- error 985
 - correction 707, 972
 - detection 704, 705
 - detection and correction (EDC) 708
 - signal 1105
- EXCLUIV-OR gate 1121
- exclusive-NOR 619
- exclusive-or 619
- expander product term 720
- exponent 643
- exponential function 745
- eye patterns 1223
- factor, distortion 187
- fall time 591, 925
- fall-through time 702
- feedback resistance 573
- feedthrough 944
- FET, junction 199
- fibre optic 1170
- field programmable gate array 691, 721
- filter 562, 1291
 - coefficient 801
 - dielectrical 1292
 - multible feedback 811
 - SAW 1242, 1291, 1300
 - single feedback 813
- finite impulse response 1224
 - filter (FIR) 996, 1015, 1300
- first harmonic wave 430
- first-in-first-out memories (FIFO) 702
- fixed-point 658

- binary number 642
- flash
 - converter 971
 - method 968
- flip-flop 593, 599, 661
- floating
 - current source 779
 - gate 708
 - gate driver 929
 - ground 1039
 - load 771
 - point 660
 - point binary numbers 642
 - point formats 643
 - point numbers 657
 - voltage 900
- flourescent lamp 1130
- flow
 - diagram 686
 - velocity 1063
- flyback
 - controller 929
 - converter 910, 918
- foldback current limiting 896
- folded cascode 366
- force 1063
- form factor 1049
- forward
 - converter 910, 920
 - gain 419
 - recovery 9
 - region 35
 - transconductance 419
 - voltage 4
 - wave 1157, 1176
- four-quadrant
 - multiplication 962
 - multiplier 757, 763
 - operation 880
- four-wire measurement 1093
- Fourier Analysis 1452
- FPGA 1463
- frequency 1169
 - compensation 511, 514
 - division duplex operation (FDD) 1237
 - division multiplex 1229
 - domain 990, 1490
 - hopping 1231
 - modulation 1193, 1204
 - multiplier 1125
 - response 158, 247, 320, 371, 552, 808, 995
 - shift keying (FSK) 1195, 1212
 - tuning 29
- frequency-sensitive phase detector 1122
- full duplex operation 1229
- full-adder 653
- full-scale error 965
- full-wave rectifier 1044
- fully compensated 519
- function
 - generator 861, 963
 - generator memories 691
 - generator network 741, 752
- fundamental wave 430
- fuse map 718

- GaAs 1323
- gain 808, 1097, 1448
 - bandwidth 574
 - bandwidth product (GBW) 126, 248, 323, 373, 517
 - control 1255, 1259
 - crossover frequency 1107
 - expansion 434
 - margin 513
- gallium-arsenide 1323
- galvanic coupling 123, 242, 268, 1254
- gate 171
 - array 691, 721
- GBW = Gain BandWidth product 323, 373, 538
- Gilbert
 - cell 758
 - mixer 1406, 1419
- glass fibre 1170
- glitch 966
- global adder 994, 1028
- gradient fibre 1173
- gray code 1218
- ground plane 572
- grounded loads 773
- group delay 798, 808, 829, 830, 992, 998, 1031, 1293
- GSM 1170
- Gummel–Poon
 - model 60, 72, 73
 - plot 39
- gyrator 561, 783

- H matrix 46
- half bridge driver 930
- half duplex operation 1229
- half-adder 651, 652
- half-band filter 1007, 1009
- half-bridge configuration 921
- half-wave rectifier 888, 1045
- hall-effect 1062
- Hamming
 - code 705
 - window 1003
- Hanning window 1003
- hardware description language 1464
- harmonic oscillator 854
- Hartley oscillator 848, 855

-
- hazards 679
 - HBT 1323
 - heat
 - flow 52
 - sink 52, 882
 - hetero-junction 1323
 - hexadecimal 1140
 - code 639
 - hidden, refresh 699
 - hierarchy 1476
 - high
 - bandwidth 585
 - current effect 16, 17, 65
 - side driver 930
 - speed DACs 968
 - high-frequency amplifiers 1323, 1329
 - high-level logic (HLL) 622
 - highpass 841
 - filter 808, 810, 814, 835, 999, 1000, 1011, 1021, 1022, 1024, 1025, 1493
 - hold
 - step 944
 - time 695
 - humidity measurement 1088
 - hybrid 1318, 1347
 - hyperabrupt doping 28
 - hysteresis 594, 604, 605

 - I/Q mixer 1430
 - IC voltage regulator 903
 - ice point correction 1076
 - ideal switch 1392
 - identity comparators 650
 - IEEE-floating-point 643
 - IF
 - filter 1251
 - sampling 1283
 - IGBT 923
 - IGFET 171
 - IIR filter 1017
 - illuminance 1129
 - image
 - filter 1249
 - frequency 1249, 1367, 1381
 - signal 1367
 - impedance 1155
 - converter 387, 769, 1033
 - matching 1303, 1310, 1312, 1324, 1334, 1339, 1340, 1361, 1412, 1426
 - transformation 148, 1303
 - impulse response 999
 - in-phase signal 1214
 - in-system programming 720
 - inductance 785
 - inductor 1285, 1288
 - infinite impulse response (IIR) 1017
 - INIC 781

 - initial
 - condition 733, 735
 - state 685
 - input
 - compensation 520
 - current 531, 574, 586
 - offset current 531
 - offset voltage 529
 - protection 574, 631
 - resistance 44, 100, 106, 112, 136, 153, 154, 419, 421, 533
 - vector 685
 - insertion gain 1358
 - instantaneous
 - amplitude measurement 1055
 - power 1505
 - instrumentation amplifier 1035
 - insulation, dielectric 195
 - integrated transistor 58
 - integrating circuit 1492
 - integrator 561, 732, 839
 - approximation 537, 538
 - inter-symbol interference 1222
 - intercept point 436, 439, 443, 1261, 1265
 - interdigital transducer 1300
 - intermediate
 - frequency 31, 1241, 1366
 - storage 663
 - intermodulation 436, 438, 1372
 - internal precision 644
 - interpolator 952, 999
 - inverse operation 62, 956
 - inverter 590
 - inverting
 - amplifier 492
 - converter 910, 916, 918
 - isolated signal transmission 1095
 - isolation
 - amplifier 1039
 - resistance 522
 - isothermal block 1074
 - ispLEVER 1461
 - iteration 1097

 - JEDEC 718
 - file 1488
 - JFET 208
 - JK* flip-flop 664
 - joint test action group 1487
 - junction
 - capacitance 19, 71
 - FET 216
 - temperature 882

 - Kaiser window 1003
 - Karnaugh map 617
 - Kirchhoff's current law (KCL) 1503

- Kirchhoff's voltage law (KVL) 1504
- ladder network 955
- large-signal analysis 1442
- latch-up 195, 631, 933
- latching circuits 589, 597, 599, 602
- latency 973
- lateral transistor 59
- LC
 - filters 1291
 - oscillator 845, 846, 849
- LCD-display 1137
- leakage
 - current 17, 64
 - inductance 919, 928
- level at a time 968
- level detection 1259
- libraries 1438, 1457, 1474
- light-emitting diode 1135
- limit
 - cycles 1031
 - data 47
- limiter 1209
- line 1160
 - isolation 929
 - receiver 636
- linear
 - phase 998, 1031
 - voltage regulator 894
- linearity error 985
- linearization 43, 415, 1066, 1115
- liquid crystal display 1138
- local oscillator 31, 1246, 1365
- logarithm 742, 1050
- logarithmic
 - power 1507
 - voltage ratio 1507
- logic
 - family 613, 637
 - function 613, 616
- logical function 637
- look-ahead carry 654
- loop gain 490, 491
- low side driver 930
- low-loss filter 1302
- low-noise 1348
 - amplifier (LNA) 1251
- lowpass filter 789, 810, 811, 815, 835, 841, 998, 1000, 1021, 1022, 1490
- lowpass/bandpass transformation 817
- lowpass/bandstop filter transformation 825
- lowpass/highpass transformation 808
- LRC*
 - bandstop filter 826
 - bandpass filter 822
 - lowpass filter 811
- luminance 1129
- luminous
 - flux 1129
 - intensity 1129
- MAC (multiply and accumulate) 1011
 - operation 1029
- macrocell 716
- MAG 1337, 1391
- magnetic
 - flux 922
 - induction 922
- magnetoresistor 1062
- magnitude 991
 - comparators 650
- mantissa 643
- manufacturers 1520
- mask-programmed ROMs 708
- master flip-flop 663
- master-slave flip-flop 663
- matching 1178
 - networks 1340
- maximum
 - available power 1391
 - available power gain 1337
 - power gain 1362
 - power point (MPP) 1133
 - received level 1264
- Mealy machine 685
- mean
 - absolute value 1044
 - noise figure 481
 - value 1493
- measurement
 - circuit 1033
 - of current 1042
 - of voltage 1033
- Meissner oscillator 847
- memories 691
- memory
 - cell 694, 708
 - matrix 696
- MESFETs 1323
- metal-oxide semiconductor 194
- metastable 681
- microstrip 1164
 - lines 635
- microwave 1170
 - filters 1298
 - integrated circuits 1331
- mid-scale glitch 966
- Miller
 - capacitance 249, 315
 - capacitor 127, 515, 518
 - effect 127, 315, 515
- minimum shift keying (MSK) 1220
- missing pulse detector 611
- mixer 15, 31, 1241, 1365

- balanced diode 1393
- conversion gain 1390,, 1429
- double balanced 1419
- down-conversion 1367
- Gilbert 1419
- I/Q 1430
- ideal 1365
- multiplicative 1378
- ring 1400
- up-conversion 1366
- unbalanced diode 1393
- voltage gain 1411, 1424
- with diodes 1383
- with transistors 1406
- modal dispersion 1173
- model 60, 199
 - of a diode 20
- modulation 1151, 1193, 1198, 1208
 - channel-length 180
 - depth 1197
 - index 1205
- modulator 1151
- modulo-counter 677
- mono-mode fibre 1173
- monostable 592, 595
- monotony error 965, 986
- Moore machine 685
- MOSFET 171
 - double diffused 196
 - integrated 194
 - model 212, 214, 217
 - power 198
 - vertical 196
 - vertical power 206
- multifunction flip-flop 667
- multiple feedback filter 811
- multiplex
 - display 1141
 - operation 1229
- multiplexer 645, 647, 932
- multiplicative mixer 1378
- multiplier–accumulator (MAC) 993
- multipliers 658, 755
- multiplying D/A converter 962
- multivibrator 596, 597, 600, 606, 607

- NAND 619
 - operation 619
 - gate 623
- negative
 - feedback 489
 - output resistance 774
 - resistance 781
- Netlist 1434, 1450
- neutralization 1342
- NIC (negative impedance converter) 736, 781
- nickel–iron thermocouple 1064

- NMOS logic 633
- noise 224, 227, 445, 539
 - current 84, 542, 587
 - current density 475
 - density 84, 445, 446
 - equivalent power 471
 - figure 89, 445, 446, 457, 541, 1261, 1263, 1282, 1326, 1348, 1349
 - gain 520
 - margin 590
 - matching 463
 - measure 454
 - rejection 981
 - shaping 982
 - shaping oversampling 982
 - source 445, 455, 540
 - voltage 84, 539, 542, 587
- noisy signal 1055
- noninverting amplifier 490
- noninverting integrator 736
- nonlinear amplifier 429
- nonlinear system 1114
- nonlinearity 103, 239, 965
- nonrecursive filter 996
- NOR
 - operation 619
 - gate 631, 633
- normal
 - mode 35, 98
 - operation 61
- normalization 274
- notch filter 825
- npn current mirror 284
- NTC thermistor 1061, 1065, 1069
- numeric aperture 1172
- numerical
 - calibration 1101
 - display 1140
- Nyquist
 - criterion 947
 - theorem 986

- octal code 638
- offset
 - binary 642, 960
 - voltage 344, 529, 531, 574, 586
- one-shot 599, 609, 682
- open
 - circuit 1179
 - line 1162
- open-collector 624, 647
- open-loop gain 824
- operating
 - point 42, 397, 409, 414, 1331, 1452
 - voltage 499, 574
- operational amplifier 485, 727
- optical transmission 1096

- optimum noise figure 449
- optocoupler 927, 1041, 1136
- optoelectronic component 1129
- orthogonal 1233
- oscillating condition 512
- oscillation test 1113
- oscillator 845
- output
 - characteristic 48
 - current 585
 - resistance 44, 100, 107, 112, 137, 153, 154, 280, 295, 421, 475, 534
 - vector 685
 - voltage 585
 - voltage control 369
 - voltage swing 494
- overdriving 573
- oversampling 951, 981

- P-controller 1106
- parallel
 - converter 969
 - method 953, 968
 - resonant circuit 1500
- parallel-T filter 827, 1499
- parallel-to-serial conversion 679
- parameter 1455
 - small-signal 184
- parameters of operational amplifiers 525
- parasitic thyristor 933
- parity
 - bit 705
 - generator 705
- partial distortion factor 433
- partially compensated 519
- Pascal 1079
- passive components 1285
- peak value 1052
- PECL-circuits 628
- phase 991, 1448
 - condition 512
 - constant 1157
 - detector 1117, 1126
 - locked loop 1116, 1202
 - locked loops, PLLs 1127, 1246
 - margin 513, 1107
 - modulation 1193
 - resonant frequency 1288
 - reversal 501
 - sensitive rectifier 1057
 - shift 808, 1490
 - shift keying (PSK) 1195
- phasor 1216
- photo-darlington 1135
- photoconductive cell 1131
- photodiode 1062, 1132
- photometric quantity 1131

- photomultiplier 1062
- photoresistor 1062
- phototransistor 1062, 1134
- photovoltaic 1133
- π attenuator 27
- PI-controller 1108
- PID-controller 1110
- piecewise approximation 747
- Pierce oscillator 852
- piezo-electric transducer 1300, 1302
- piezoresistive pressure sensor 1087
- pilot channel 1215
- pin
 - assignment 1477
 - diode 13, 27
- pinch-off current source 408
- pipeline ADC 973
- platinum temperature sensor 1064, 1069
- PLD 637, 1461, 1463
- PLL 1116, 1246
 - demodulator 1211
- point, operating 183, 245
- polar to Cartesian 765
- pole splitting 515
- post layout simulation 722
- potential 1502
 - difference 1034
 - shift 494
- power 1505
 - amplifier 869
 - bandwidth 518
 - consumption 873
 - derating 50, 53
 - dissipation 12, 49, 635, 872, 909
 - driver 929
 - efficiency 1220
 - factor 1506
 - function 746
 - gain 1337, 1345, 1349, 1356, 1357
 - MOSFET 923, 925
 - on reset 685
 - rectifier 888
 - series expansion 749
 - splitter 1317
 - supply 887, 909
 - switch 923
 - transformer 887
 - transmission factor 1178
- precision current source 774
- pressure 1063
 - measurement 1078
 - sensor 1087
- primary switching regulator 918
- priority decoder 648
- probe 1434, 1441
- product term sharing 720
- programmable

- counter 686
- interconnect matrix 721
- logic array 691
- logic devices (PLDs) 691, 713
- ROMs (PROMs) 708
- programming 1486
- project navigator 1462
- propagation constant 1157
- propagation delay time 591
- proportional to the absolute temperature (PTAT) 1071
- pseudo random binary sequence (PRBS) 1236
- PSpice 1433
- PTC thermistor 1061, 1064, 1067
- pull-in 1120
- pulse
 - shaping 1221
 - transformer 927
- pulsewidth modulator 913, 926
- push–pull 592, 871
 - controller 929
 - converter 920, 926
 - differential amplifier 510
 - oscillator 850
- pyroelement 1062
- pyrometer 1062

- Q -factor 818, 833
- QPSK modulator 1226
- quadrature
 - amplitude modulation (QAM) 1195, 1221
 - signal 1214
- quadrature-phase shift keying 1220
- qualifiers 684
- quality factor 1288, 1291
- quantization
 - error 985
 - noise 952, 981
- quartz crystal 851
- quasi-complementary 877

- radiation 1165
 - efficiency 1168
 - resistance 1167
- radio 1165
 - frequency 1366
 - link 1168
- rail-to-rail 500, 575
 - amplifiers 502
 - input-output (RRIO) 585
 - output (RRO) 967
- random access memory 691, 692
- reactive power 1506
- read only memory (ROM) 691, 708
- read-while-write memory 700
- receiver 1151, 1247, 1274
 - diode 1171
 - direct conversion 1279
 - direct detection 1246
 - for digital modulation 1267
 - gain 1168
 - signal strength indicator (RSSI) 1260
 - superheterodyne 1249, 1250, 1252
 - with two intermediate frequencies 1252
- receiving efficiency 1168
- recombination
 - current 16
 - region 17
- reconstruction 951
- rectifier diode 3
- reduced transconductance 129
- reference
 - junction 1074
 - junction compensation 1077
 - point compensation 1076
 - signal 1105
 - voltage 895, 903
 - current source 398, 408
 - current source PTAT 402
- reflected wave 1157, 1176
- reflection
 - coefficient 1176, 1177, 1186
 - factor 1287, 1334
- refraction 1172
- refresh 697
- region
 - ohmic 174
 - pinch-off 174, 184
 - saturation 174
 - sub-threshold 203, 218, 235
- rejection filter 825
- relative humidity 1088
- Remez Exchange Algorithm 1002, 1018
- resistance 1502
 - output 185
 - spreading 205
- resistor 1285, 1286
- resistor-transistor logic (RTL) 621
- resolution 952, 988
- resonant circuit 1500
- resonant frequency 1288
- resonator 1298
- retriggerable timer 610
- reverse
 - current 5, 11, 38, 47
 - gain 418
 - recovery charge 9
 - recovery time 9
 - region 4, 35
 - transconductance 45, 419
 - voltage 11
- RF
 - filter 1249
 - sampling 1283

- Richards transformation 1298
- ring
 - coupler 1318
 - memory 702
 - modulator 31, 1397
 - shifter 650
- ripple carry 653
 - counter 669
 - output (RCO) 670
 - voltage 889
- rise time 591, 925, 1493
- rms value 1048
- rod antenna 1167
- roll-off factor 1221
- ROM 637
- root-mean-square 1048
- route 722
- row
 - address strobe 696
 - decoder 693, 696
- RRIO 585
- RS flip-flops 662, 680
- S
 - matrix 1185
 - parameter 1176, 1185, 1188, 1191, 1338, 1356
- safe operating area (SOA) 50, 190, 895, 924
- sample-and-hold 943, 1053, 1118
- sampling
 - frequency 988
 - theorem 947, 948, 986
- saturation 432, 925
 - humidity 1088
 - mode 99
 - region 35
 - reverse current 16
 - voltage 62
- SAW filter 1242, 1291, 1300
- SC
 - filter 839, 843
 - integrator 838
- scaling 274
- scattering parameter 1185
- schematic 1434, 1472
 - editor 1472
- Schmitt trigger 594, 597, 603, 604, 606, 861
- Schottky 3
 - diode 14, 15, 936
 - TTL 624
- second harmonic wave 430
- secondary breakdown 48, 924
- self-resonating frequency 1288, 1290
- sensitivity 1264
- sensor 1061
 - terminal 901
- sequential circuit 684
 - logic 661
 - logic circuits 637
- serial-to-parallel conversion 679
- series
 - connection of amplifiers 423
 - regulator 908
 - resonant circuit 1500
 - switch 931, 938
 - /short switch 931, 939
- setting time 944
- seven-segment
 - decoder 1140
 - display 1140, 1147
- shielded line 1154
- shift register 678, 700
- short circuit 1179
 - channel 200
 - circuit output resistance 415
 - circuiting switch 931, 938
 - line 1162
- shot noise 86
- shunt regulator 908
- sideband 1197
- SiGe 1323
- sign
 - extension 641
 - reversal 1046
- signal
 - flow graph 741
 - generator 845
 - processor 1029
 - transmission 636
- signal-to-noise ratio 481
- signed-magnitude representation 639
- silicon-germanium 1323
- simulation 1434, 1481
- simulator 718
- sine
 - wave 861
 - function 747
- single
 - balanced mixer 1406
 - bit error 706
 - feedback filter 813
 - precision 644
 - supply 499
- single-ended converter 919
- single-mode fibre 1173
- single-slope converter 978
- single-supply amplifier 500
- 16-segment display 1144, 1147
- size
 - electrical 274
 - geometrical 274
- skin effect 923, 1288
- slave flip-flop 663
- slew rate 517, 519, 943

- limiter 1116
- slope detector 1209
- small-signal 10, 43, 184
 - characteristics 414
 - equivalent 10
 - gain 416
 - input resistance 415
 - model 22, 76
 - output resistance 415
 - parameter 43, 84, 415, 420
 - response 41, 100
 - value 414
- SMD 1285
- smoothing factor 25
- solar cell 1133
- source 171
 - follower 254
- special diode 24
- spectrum analyzer 1059
- speed-up diode 925
- spread spectrum modulation 1231
- spreading resistance 6, 18, 70, 96
- square
 - rooter 764
 - wave 861
- stability factor 1336
- stabilization factor 25
- stable power gain 1363
- staggered tuning 820
- staircase function 950
- standard
 - operational amplifier 486
 - series 1517
- standing wave 1182
- state 835
 - diagram 684, 686, 1123, 1464, 1471
 - vector 685
- static
 - error 535, 965, 985
 - losses 927
 - nonlinearity 1114
 - RAM 692
- step response 992
- step-down converter 910, 914, 918
- step-index fibre 1173
- step-response 1992, 491
- step-up converter 910, 915, 918
- steradian 1129
- storage time 591, 925
- straight binary code 638
- strain gauge 1063, 1079
- strip line 1164, 1309
- stub lines 1311
- subsampling 1274
- substrate 15, 35
 - capacitance 79
 - control factor 192, 201
 - diode 15, 68
 - effect 503
 - transconductance 218
- subtracting
 - amplifier 729
 - circuit 728
- subtraction 656
- subtractor 1034, 1036
- successive approximation 974
 - register (SAR) 976
- sum 652
- summing
 - amplifier 727
 - integrator 736
- superheterodyne receiver 1249, 1250, 1252
- supply voltage 364
- surface
 - acoustic wave filters (SAW) 1224, 1300
 - mounted devices 1285
- sweep 1453
- switch 932
- switchable gain 942
- switched
 - capacitor filter 838
 - current source 958
- switched-capacitor 1039
 - technology 1091
- switched-mode 909
- switching 8
 - converter 918
 - time 596
- symbol
 - duration 1221
 - rate 1218
- symmetrical limitation 26
- synchronization 681
- synchronous
 - clock switch 683
 - counters 669
 - demodulator 1055, 1057, 1120, 1202
 - edge detector 683
 - one-shot 682
- syndrome generator 706
- system ground 1039

- table memories 691
- tautology 613
- Taylor series 428
- telecommunication 1151
- temperature
 - coefficient 24, 906
 - compensation 192, 235, 1086
 - measurement 1061
 - sensitivity 12, 103
 - sensor 1078
 - tolerance 1065
 - voltage 6

- temperature-compensated pressure sensor
 - 1081, 1084
- temporary state 685
- termination 1161, 1162
- text vectors 1481
- thermal
 - capacity 51, 52
 - conversion 1051
 - equivalent 52
 - noise 85
 - protection 895
 - resistance 51, 52, 882
 - voltage 742
- thermocouple 1073, 1075
- 35-segment display 1147
- three-wire measurement 1093
- thyristor 631
- time division
 - duplex operation (TDD) 1237
 - multiple access 1229
- time-domain 990, 1491
- timer 608
- timing 695
 - analysis 1485
 - simulator 719
- toggle flip-flops 666
- total nonlinearity 986
- tracking A/D converter 978
- transadmittance 82
- transconductance 44, 83, 178, 179, 184, 416
 - amplifier 487, 542, 544, 940
 - cutoff frequency 221
 - divider 761
 - multiplier 756, 760
 - reduced 250, 352
- transfer
 - characteristic 412, 624
 - function 807, 990, 991
 - gain 1359
 - resistance 154
- transformation 1163, 1304, 1310
 - of coordinates 765
- transformer 95, 463, 922, 1162
- transient 1442
- transimpedance amplifier 151, 487, 488, 546
- transistor
 - as switch 589
 - as temperature sensor 1070
 - field effect 171
- transistor–transistor logic (TTL) 623
- transit
 - frequency 80, 221, 222
 - time 20, 73
- transmission
 - channel 1154
 - coefficient 1186
 - efficiency 1168
 - equation 1157
 - gate 631, 632, 648, 933
 - line 1160
 - of sensor signal 1092
- transmit gain 1168
- transmitter 1151, 1239
 - with digital modulation 1245
 - with diode 1171
 - with direct modulation 1239
 - with one intermediate frequency 1241
 - with two intermediate frequencies 1242
 - with variable transmission frequencies 1244
- transparent flip-flops 661
- transport model 60, 63
- transversal filter 996, 1300
- triangular wave 861, 1049
- triple-transit echo 1300
- tristate 647
 - output 626
- true rms 1049
- truth table 616, 637, 1471
- TTL 624, 719
 - library 1475
 - modules 1475
- tuning diode 28
- turn-on time 595
- twisted pair 1155
- two step converter 971
- two's complement 640, 656, 960
- two-pole frequency compensation 524
- two-port memories 699
- two-wire
 - current loop 1094
 - line 1154
- UMTS 1170
- undersampling 1011
- unilateral power gain 1363
- unsaturated logic 591
- unshielded 1154
- up–down counter 671
- up-conversion 1365
- up-counter 668
- uplink 1234, 1266
- varactor diode 28
- variable
 - capacitance diode 3
 - filter 835
 - gain amplifier (VGA) 1255, 1257
- varicap 28
- vector
 - magnitude 766
 - sum 1058
- velocity of propagation 1155
- vertical transistor 58

- VHDL 719, 1462
- virtual ground 492
- voltage 1502
 - biasing 118
 - breakthrough 188
 - common-mode 372
 - controlled oscillator VCO 598
 - differential 372
 - divider 1496
 - early 181, 201, 208
 - feedback 109, 113, 241, 251, 468, 470, 1331
 - feedback operational amplifier 486
 - flat-band 192
 - follower 1034
 - gain 100, 105, 111, 136, 153
 - inversion 192, 201
 - limitation 26
 - pinch-off 172
 - source 1502
 - stabilization 25, 905
 - threshold 172, 201, 208
- voltage-controlled
 - current source 771
 - oscillator (VCO) 1116, 1126, 1208
 - voltage source 769
- voltage-to-duty factor conversion 1096
- voltage-to-frequency conversion 1096
- VSWR 1182
- VV operational amplifier 494

- wafer 13
- wait state 685
- Wallace tree 659
- Walsh code 1233
- wave
 - length 1157
 - parameter 1176
- waveform viewer 1483

- waveguide 1171
- weighting method 953, 968
- Wheatstone bridge 1079
- white noise 85, 445, 449, 1049
- wideband
 - full-wave rectifier 1047
 - multiplexer 941
 - operational amplifier 506
- Widlar current mirror 288
- Wien–Robinson
 - bandstop filter 827
 - bridge 1497
 - oscillator 855
- Wilkinson splitter 1318
- Wilson current mirror 304
- window
 - comparator 603
 - method 1002
- wired-AND 625
- wired-OR 625
- wires 1440
- word at a time 968
- write cycle time 695

- Y
 - matrix 46, 186
 - parameter 223, 1188
- Yulewalk Algorithm 1018

- Z-transform 991
- Zener
 - diode 3, 24, 895, 903
 - effect 24
 - voltage 24
- zero
 - point 1097
 - point error 965
 - power 720
 - voltage switching 929